 


Computer Architecture Lab


Lab04 – Week #4

MUX using Transmission Gate




- You should consider Transmission gate's feature and MUX's function
- Input 1 goes output when $S = 1$
- Input 2 goes output when $S' = 1$

Latch using MUX

 


- You should consider The function of the latch storing the value
- You should consider the number of MUX's input
- Based on D latch, the number of input is two, D and enable
- It is important how to connect the remaining input to keep the values stored

D-Flip Flop using Latch

 


- It is easy to design considering the form of Master-slave D-Flip Flop
- FF design uses the method of Latch design with Mux
- When connecting the input, you should consider that master's output enters slave's input
- Master operates when clock is 1, and slave operates when clock is 0

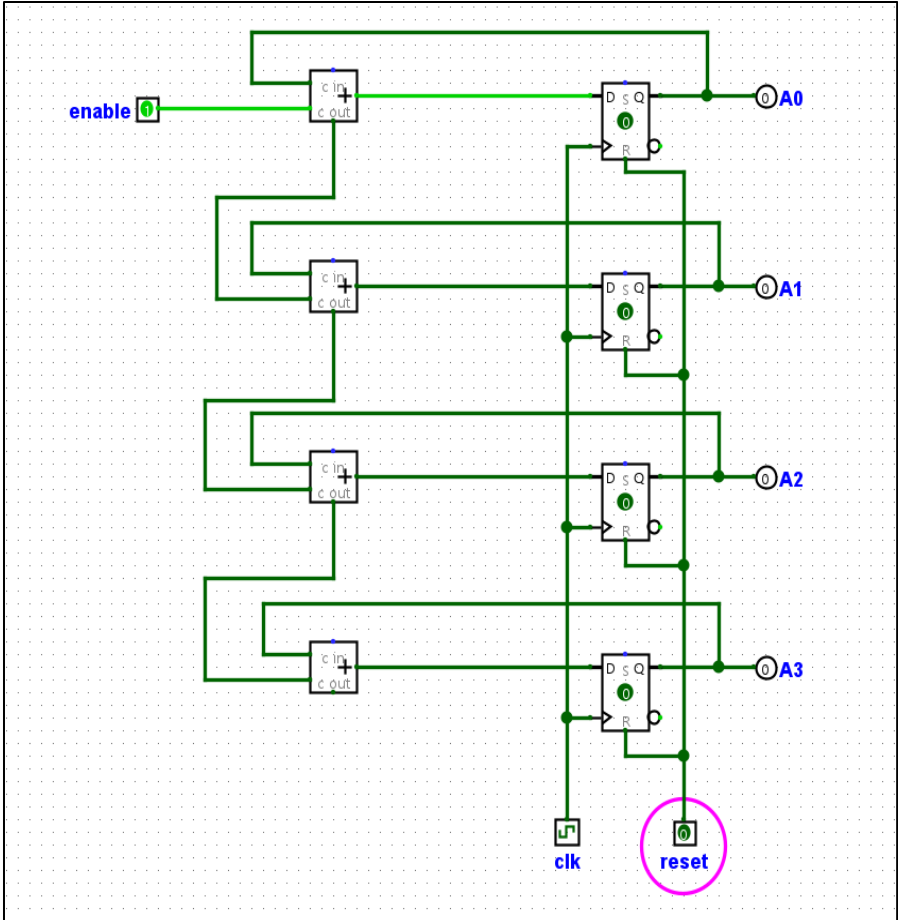
- You should consider pushing up the value through `c_in` and `c_out` of the Adder



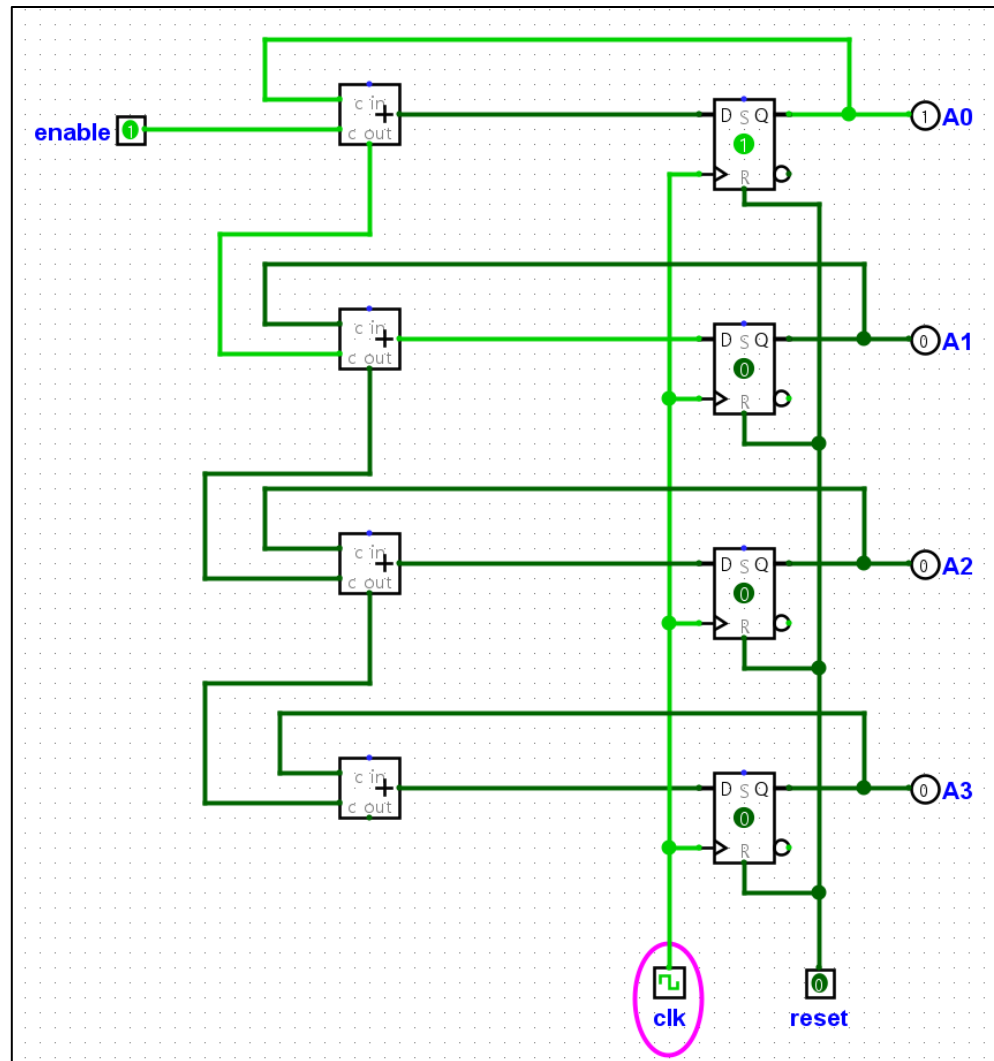
Synchronous Up-Counter Using D-FF&Adder (2/5)



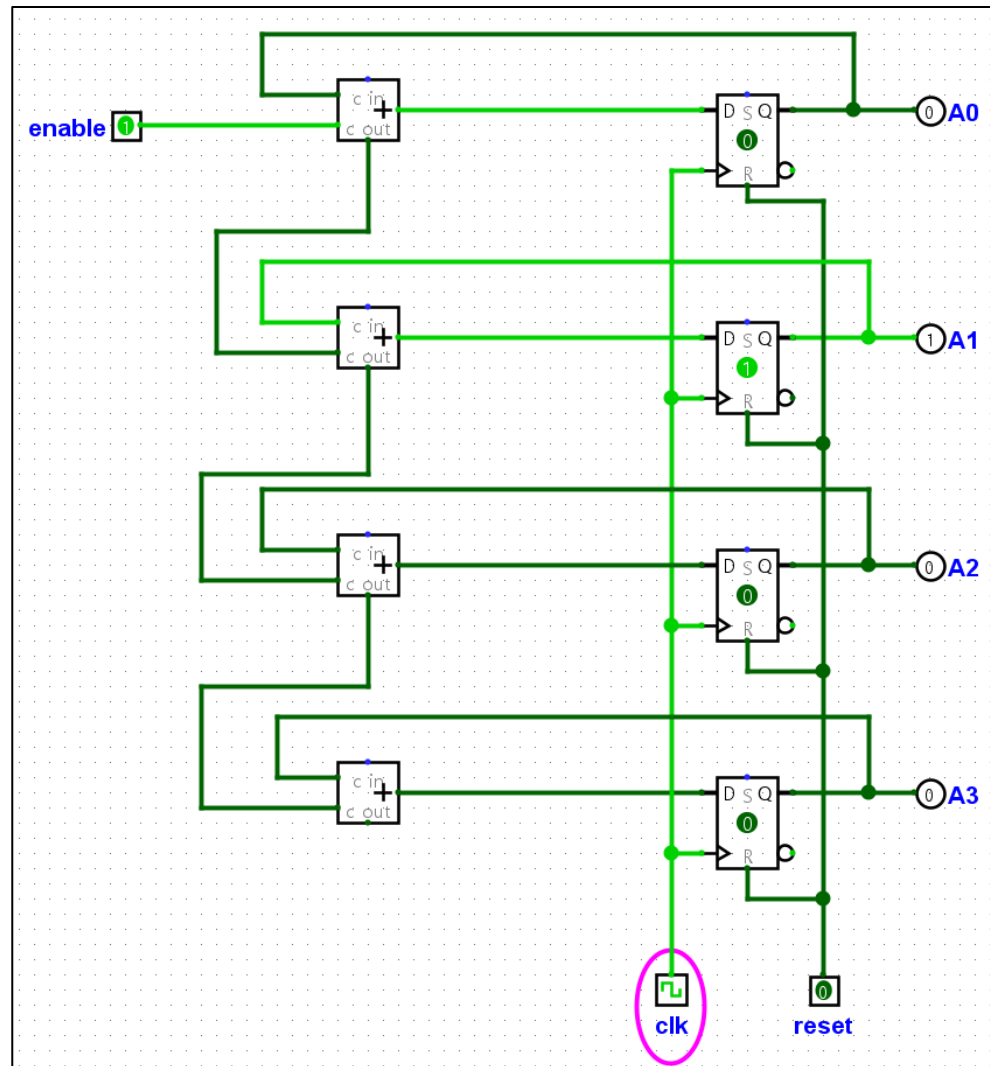Synchronous Up-Counter Using D-FF&Adder (3/5)




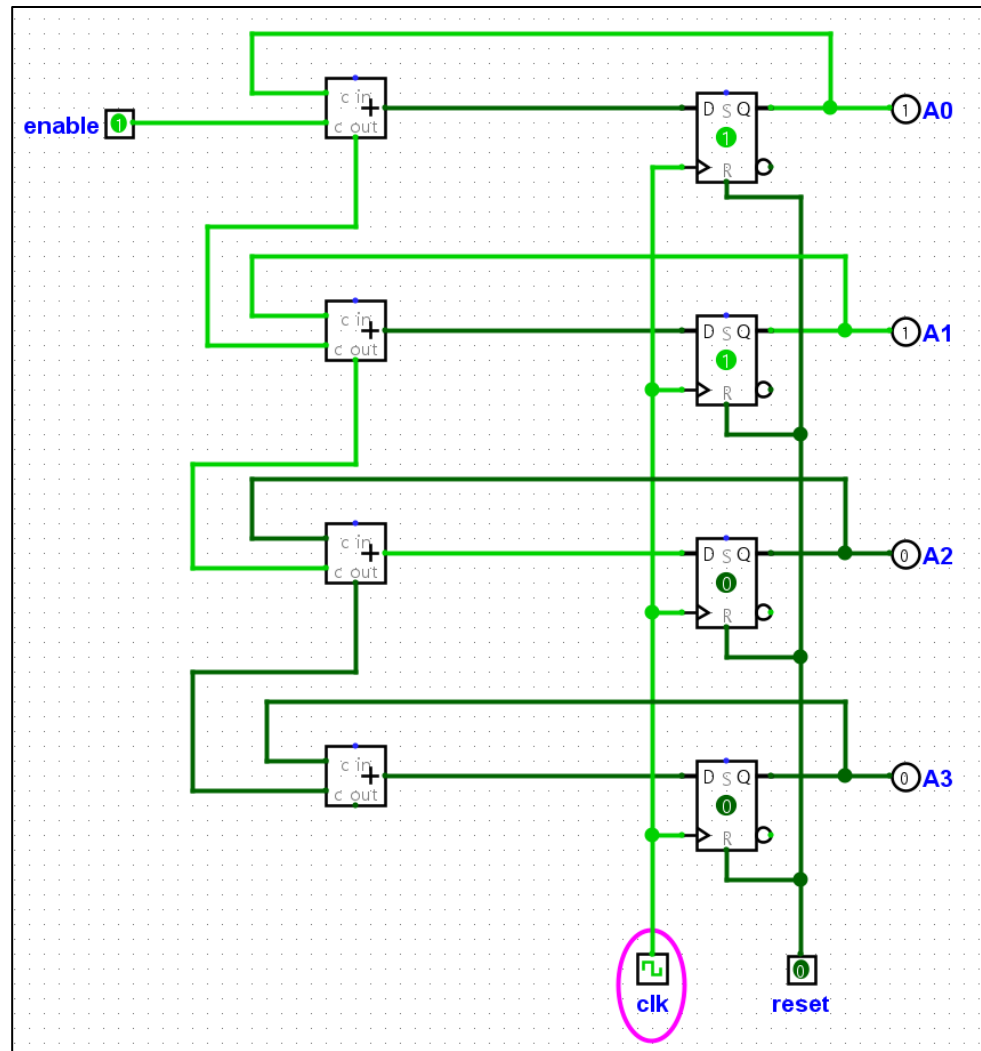Synchronous Up-Counter Using D-FF&Adder (4/5)



Synchronous Up-Counter Using D-FF&Adder (5/5)

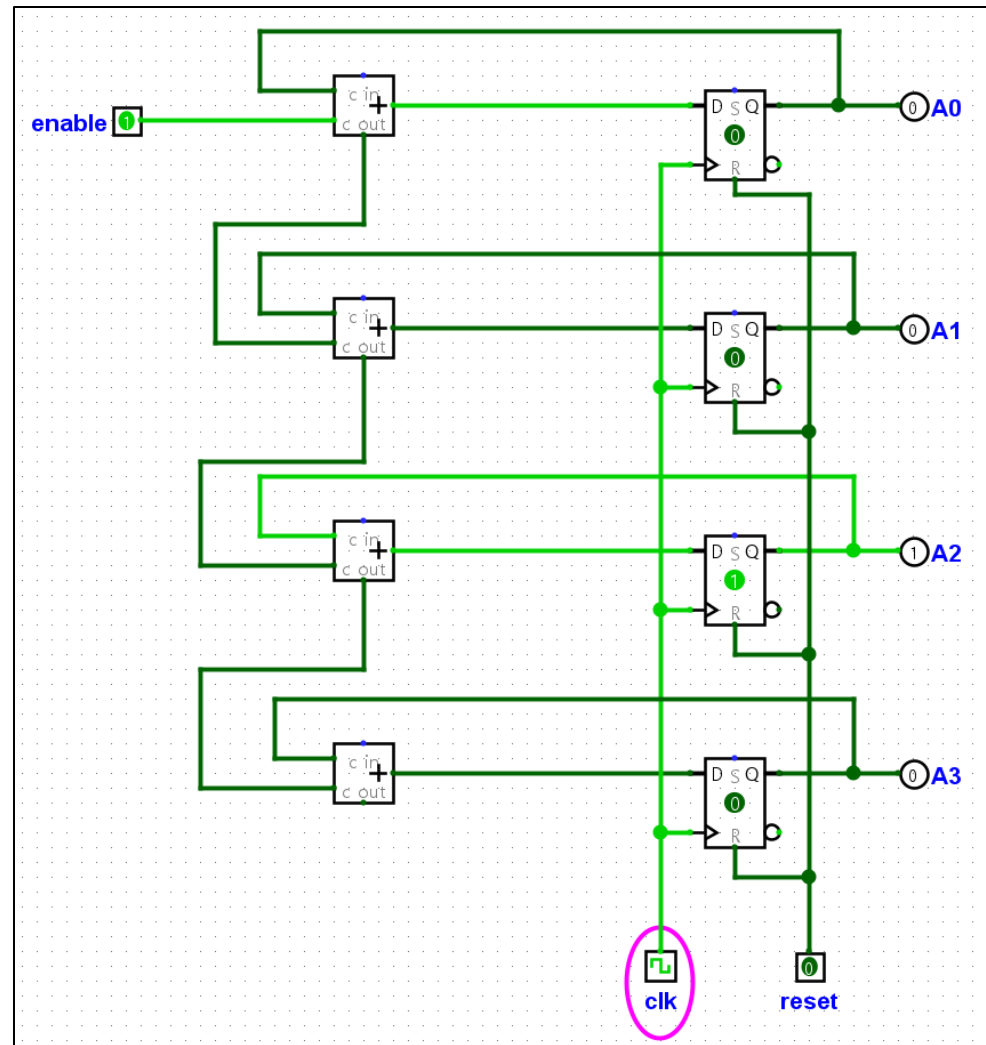
- When you have to design Synchronous up-down counter, recommend to use mux to control input value
- Point is to use c_in



MU0 Instructions


- op-code 0000 (LDA S): **load into accumulator**, operand from memory location addressed as 'S'
- op-code 0001 (STO S): **store** the content of accumulator register at the **memory location addressed as 'S'**
- op-code 0010 (ADD S): **$ACC = ACC + [S]$** add content of memory location addressed as 'S' with content of accumulator and save result at accumulator
- op-code 0011 (SUB S): **$ACC = ACC - [S]$**
- op-code 0100 (JMP S): **jump** to the memory location addressed as 'S'. This will unconditionally change the program flow. **$PC = [S]$**
- op-code 0101 (JGE S): **if $ACC \geq 0$** , then jump.
This is conditional jump with condition that ALU result is positive
- op-code 0110 (JNE S): another conditional jump with condition that **ACC content is non-zero**
- op-code 0111 (STP): **stop** the program execution

MU0 Processor

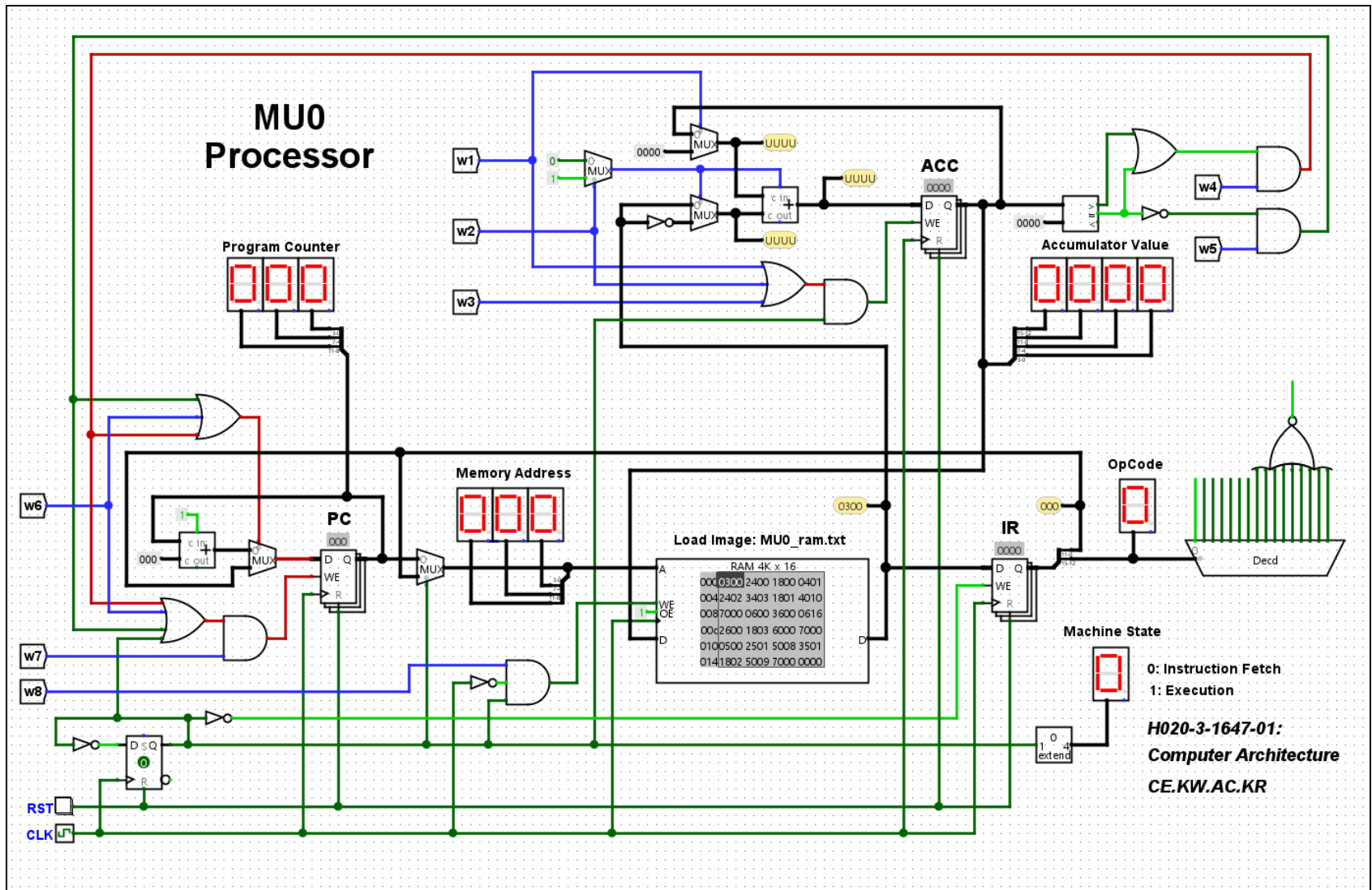


Ex) Load (1/3)

➤ Fetch

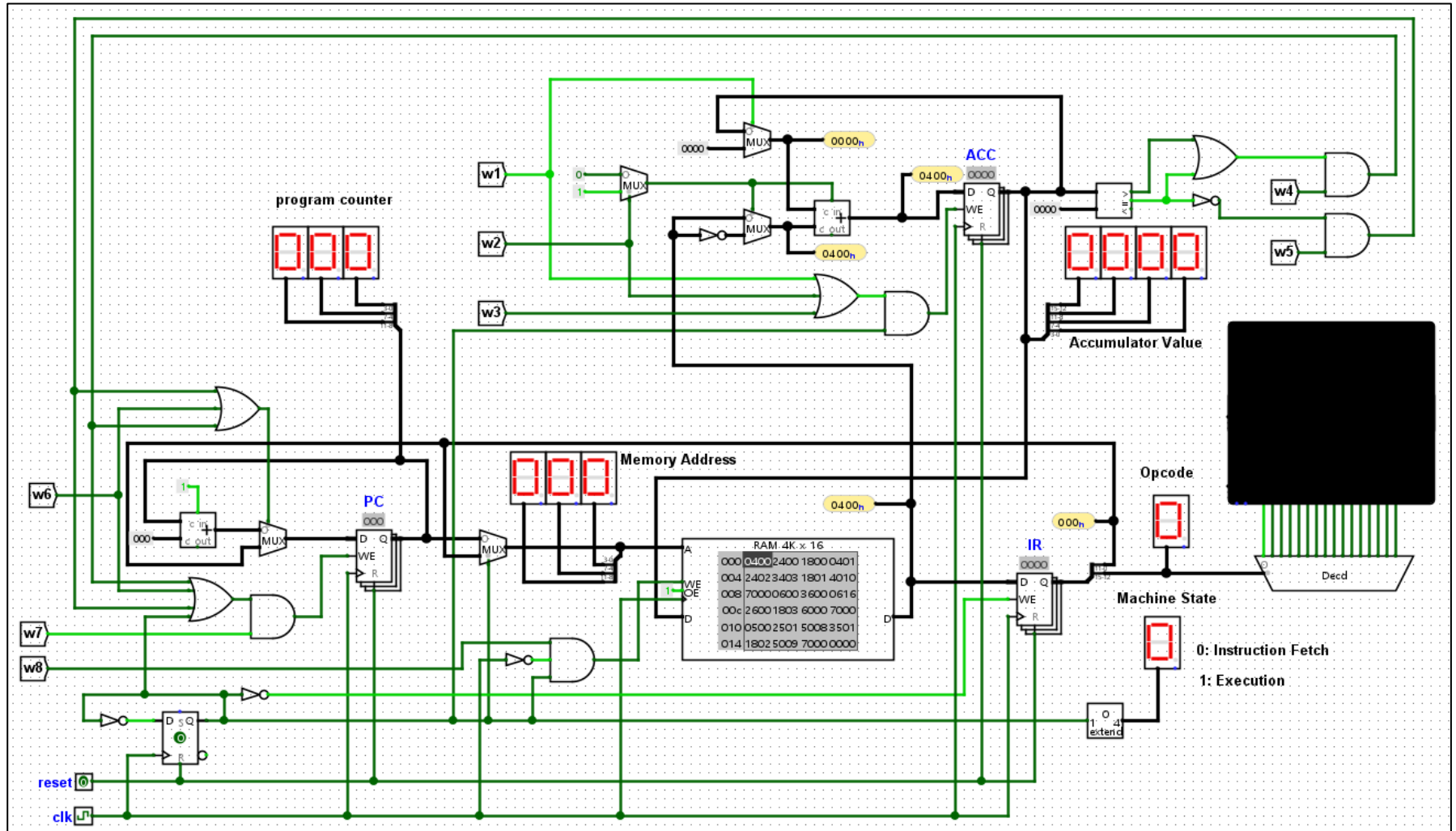


Ex) Load (2/3)

➤ Execution

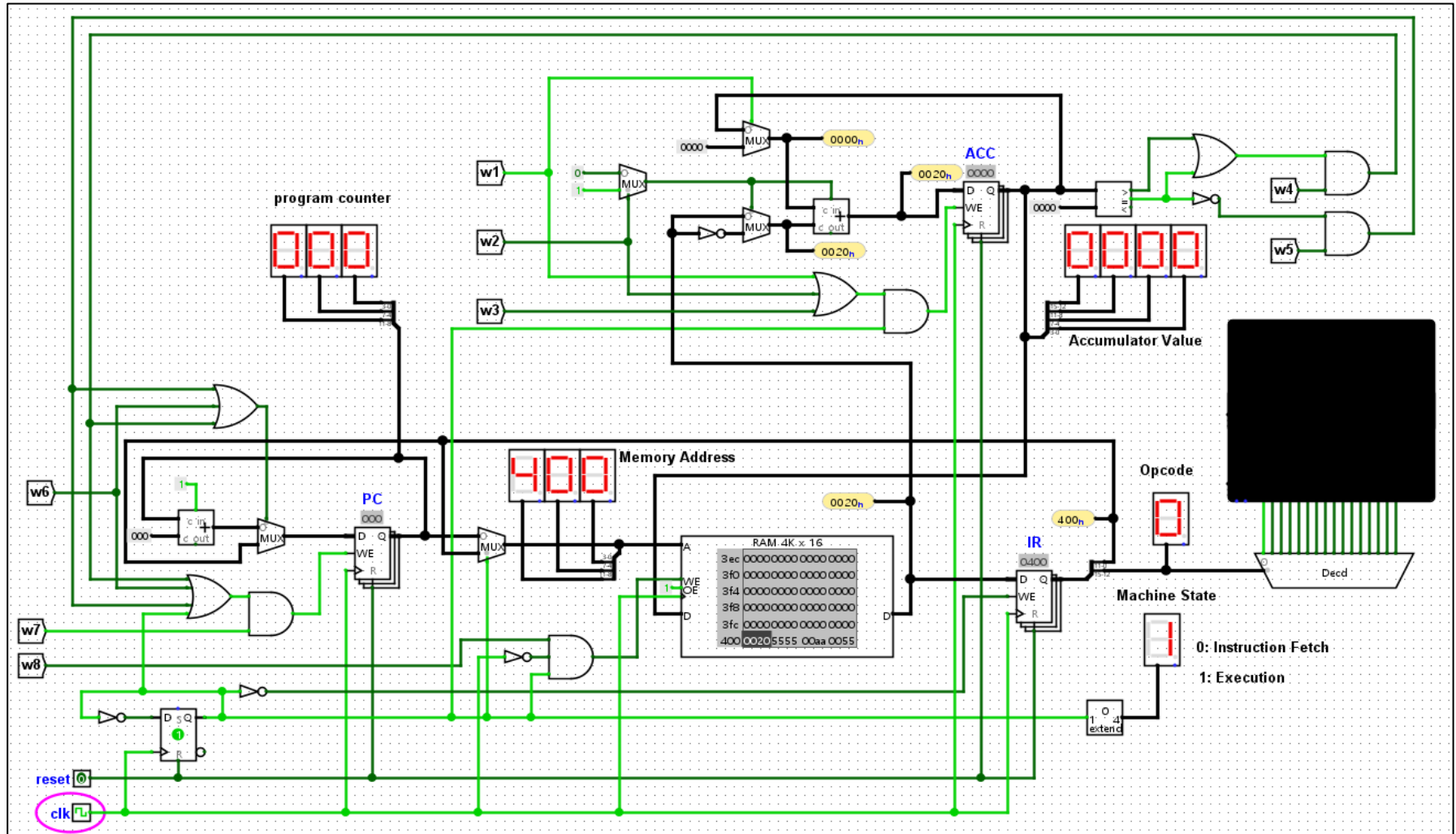


Ex) Load (3/3)


➤ Next Fetch

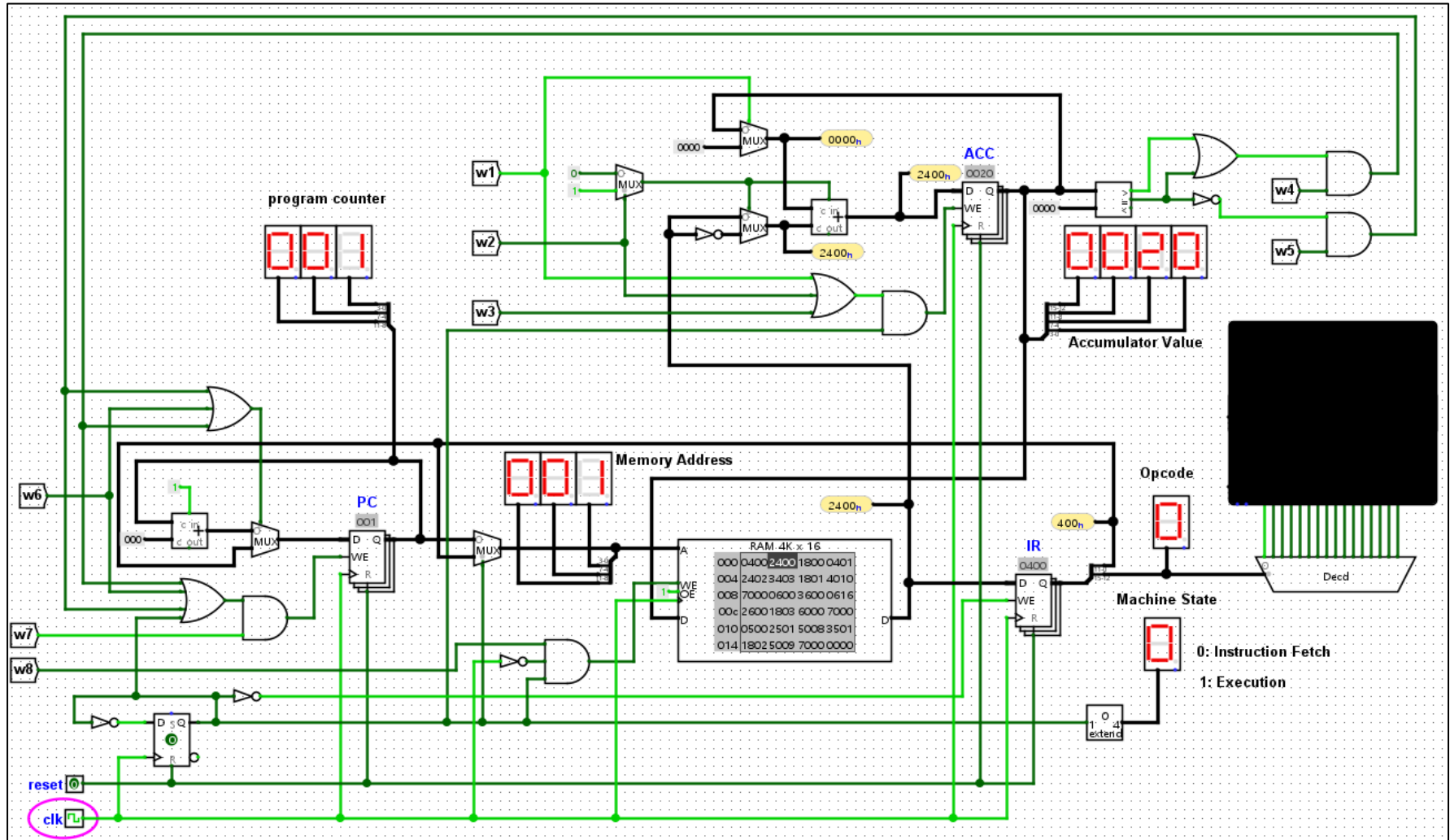


How to use MU0.txt

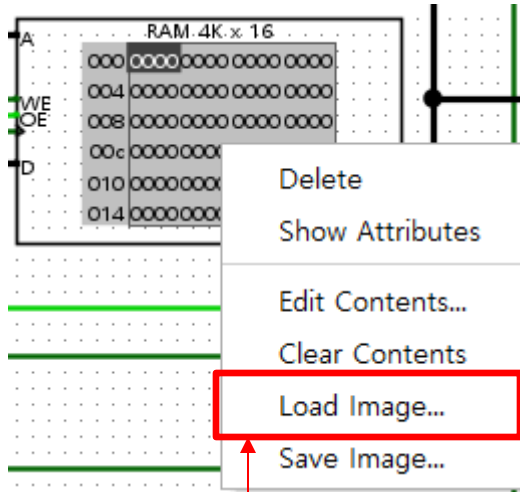

Click!

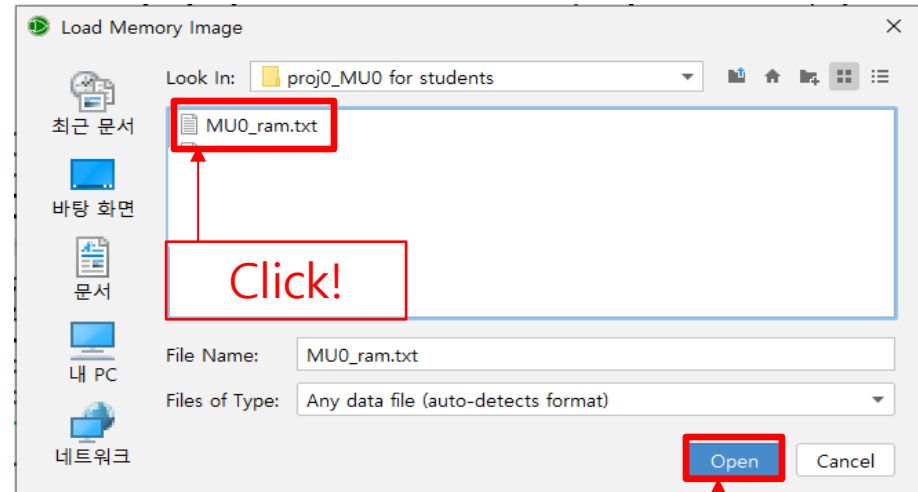

Click!

 


Loaded


Point to note

- Be careful of ram settings
- Be careful of number of bits
- You can also change appearance

✓ Logisim-evolution

 

✓ Classic logisim

 

✓ RAM

RAM (800,650)	
FPGA supported:	Not supported
Address Bit Width	12
Data Bit Width	16
Enables:	Use byte enables
Ram type	volatile
Use clear pin	No
Trigger	Rising Edge
Asynchronous read:	Yes
Read write control	Whole word read/write only
Data bus implementation	Separate data bus for read and wr...
Label	HDL Required
Label Font	SansSerif Bold 16
Label Visible	No
Appearance	Classic Logisim

Thank You