
# Computer Architecture Lab

Lab05 – Week #5

 

# Single Cycle CPU\_ex.subu





# Single Cycle CPU module

 


Table 1 - Instance name of top module

Instance name	Description
SC_CPU	Top module. Single-Cycle CPU
U0_PC	Program counter
U1_IM	Instruction memory
U2_RF	Register file
U3_SEU	Sign Extension Unit
U4_ALU	Arithmetic Logic Unit
U5_MULT	Multiplier Logic Unit
U6_DM	Data memory
U7_CTRL	Control unit -MainControl, MyControl



### PLA\_AND.txt

Table 2 - Consecutive Instruction Decoding Configuration in PLA\_AND.txt

Port name	Classification	Bit	Description
Ор	Input	6-bit	Op code
Func	Input	6-bit	Function code
Regimm	Input	5-bit	Register Immediate code (RT)



R-Type:

I-Type:

J-Type:

ор	\$rs	\$rt	\$rd	shamt	func
ор	\$rs	\$rt		imm16	
ор			imm26		



#### PLA\_AND.txt

- R-type's opcode is 000000
- When implementing R-type instructions, you should fill Function
- Regimm is filled when you implement specific I-type instructions (ex.bltz, bgez)

Reglmm	(I-Type) w	/ith \$rt:						
Ħ	000	001	010	011	100	101	110	111
00	bltz	bgez	bltzl	bgezl				
01	tgei	tgeiu	tlti	tltiu	teqi		tnei	
10	bltzal	bgezal	bltzall	bgezall			·	
11								

subu	100011	f \$d, \$s, \$t	\$d = \$s - \$t
------	--------	-----------------	-----------------

```
xxxxxx_xxxxxx_xxxxx // 0x00 : sll
xxxxxx xxxxxx xxxxx // 0x01 : srl
xxxxxx xxxxxx xxxxx // 0x02 : sra
xxxxxx_xxxxxxx_xxxxxx // 0x03 : sllv
xxxxxx xxxxxx xxxxx // 0x04 : srlv
xxxxxx_xxxxxxx_xxxxx // 0x05 : srav
xxxxxx_xxxxxxx_xxxxx // 0x06 : jr
xxxxxx_xxxxxx_xxxxx // 0x07 : jalr
xxxxxx_xxxxxx_xxxxx // 0x08 : break
xxxxxx_xxxxxx_xxxxx // 0x09 : mfhi
xxxxxx_xxxxxx_xxxxx // 0x0a : mthi
xxxxxx_xxxxxx_xxxxx // 0x0b : mflo
xxxxxxx_xxxxxxx_xxxxxx // 0x0c
                               mtlo
                               mult
xxxxxx_xxxxxxx_xxxxxx // 0x0d
xxxxxx_xxxxxxx_xxxxx // 0x0e multu
xxxxxxx_xxxxxxx_xxxxxx // 0x0f
                              div
Opcode_Function Regimm
```



# PLA\_OR.txt


Table 3 - Consecutive Control Signal Configuration in PLA\_OR.txt

Port name	Classification	Bit	Description
RegDst	Output	2-bit	Register Control signal
RegDatSel	Output	2-bit	Register Write Data Selection signal
RegWrite	Output	1-bit	Register Control signal
SEUmode	Output	1-bit	Extender Control signal
ALUsrcB	Output	2-bit	ALU Input Selection signal
ALUctrl	Output	2-bit	ALU Control signal
ALUop	Output	5-bit	ALU Operation Control signal
DataWidth	Output	3-bit	Memory Data Control signal
MemWrite	Output	1-bit	Memory Control signal
MemtoReg	Output	1-bit	MEM/ALU Selection signal
Branch	Output	3-bit	Branch Address Control signal
Jump	Output	2-bit	Jump Address Control signal

<sup>\*</sup> The last 5 bits are reserved. Set them as xxxxx.



#### PLA\_OR.txt

 



#### M\_TEXT\_SEG.txt

■ M\_TEXT\_SEG.txt - Windows 메모장

00000000\_01100101\_00110000\_00100011

//lui \$0 \$2 0x1234 lui : load upper immediate //ori \$2 \$3 0x5678 ori : or immediate //lui \$4 0x1122 //ori \$5 \$4 0x3344

\*You can change underbar(\_) position for convenience

R-Type:


I-Type:


J-Type:

ор	\$rs	\$rt	\$rd	shamt	func
ор	\$rs	\$rt		imm16	
ор			imm26		



#### Simulation (1/7)

 


 






#### Simulation (2/7)

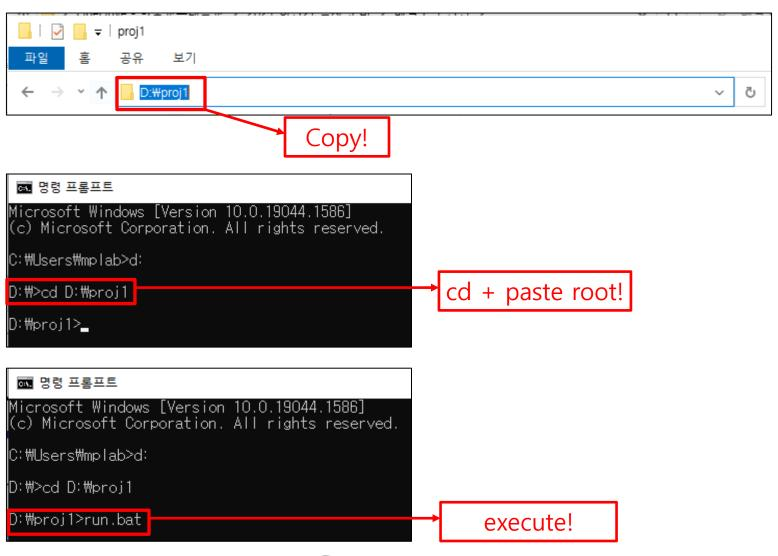




#### Simulation (3/7)

 




#### Simulation (4/7)

 





#### Simulation (5/7)

 




#### Simulation (6/7)

 

 



# Simulation (7/7)

 



# Thank You